

# COLLEGE OF ENGINEERING, PUNE

(An Autonomous Institute of Government of Maharashtra.)  
SHIVAJI NAGAR, PUNE - 411 005

## END Semester Examination

### ET-201- Electronic Devices and Circuits

Course: B.Tech

Branch: Electronics and TeleCommunication Engineering

Semester: Sem III

Year: 2014-2015

Max.Marks:60

Duration: 3 Hours Time:- 10.00 am to 1.00pm

Date:30/11/2014

#### Instructions:

MIS No.

--	--	--	--	--	--	--	--	--	--

1. Figures to the right indicate the full marks.
2. Mobile phones and programmable calculators are strictly prohibited.
3. Writing anything on question paper is not allowed.
4. Exchange/Sharing of anything like stationery, calculator is not allowed.
5. Assume suitable data if necessary.
6. Write your MIS Number on Question Paper

- Q.1 a) State Mass Action law and explain it in detail. [4]
- b) In a P-type semiconductor, the Fermi-level lies 0.4eV above the valence band. If the concentration of acceptor atoms is tripled, find the new position of Fermi-level. Assume  $kT = 0.03eV$  [3]
- c) What are the two types of capacitances across a P-N Junction? Explain them in detail. [4]
- d) The reverse saturation current of a silicon diode is 5 mA at room temperature. Find the diode current at [4]
- i)  $40^{\circ}C$  and forward voltage of 0.3 V,
  - ii)  $60^{\circ}C$  and a forward voltage of 0.5 V. Assume  $\eta = 2$ .
- Q.2 a) Draw the drain and transfer characteristics of p-channel D-MOSFET. [2]
- b) For the circuit shown in figure 1, find [5]

- i)  $I_{DQ}$
- ii)  $V_{GSQ}$
- iii)  $V_{DS}$
- iv)  $V_D$
- v)  $V_S$

Given:  $I_{D(on)} = 5 \text{ mA}$  at  $V_{GS} = 6 \text{ V}$  and  $V_{GS(Th)} = 3 \text{ V}$ .

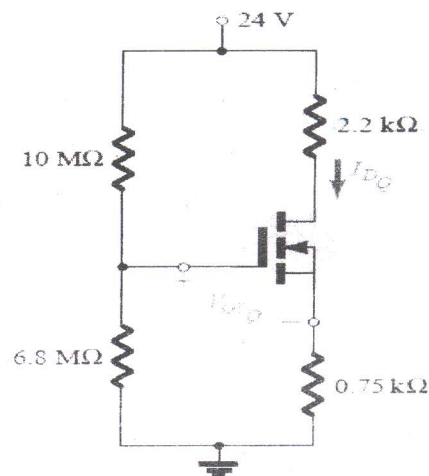


Figure 1

b] With the help of neat diagram explain different current components in BJT. Define  $\alpha_{dc}$  and  $\beta_{dc}$  and derive relation between them. [5]

c] A DC analysis of network in figure 2 will result in  $V_{GSQ} = -2.2$  V and  $I_{DQ} = 2.03$  mA [8]

- i) Determine  $g_m$ .
- ii) Find  $r_d$ .
- iii) Determine  $Z_i$  with and without  $r_d$ . Compare results
- iv) Calculate  $Z_o$  with and without  $r_d$ . Compare results
- v) Determine  $V_o$  with and without  $r_d$ . Compare results

Given:  $I_{DSS} = 10$  mA,  $V_P = -4$  V and  $y_{os} = 50$   $\mu$ S

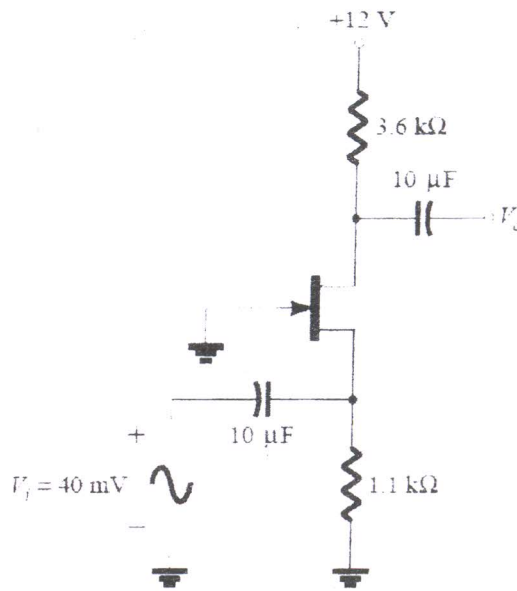


Figure 2

Q.3 b] The amplifier shown in figure 3 uses a transistor with the following parameters:  $h_{ie} = 1.1$  k $\Omega$ ,  $h_{fe} = 50$ ,  $h_{re} = 2.5 \times 10^{-4}$  and  $h_{oe} = 25 \times 10^{-6}$   $\mu$ A/V. Calculate: [9]

- i)  $A_i$
- ii)  $A_{IS}$
- iii)  $A_V$
- iv)  $A_{VS}$
- v)  $R_o^1$  and  $R_i^1$

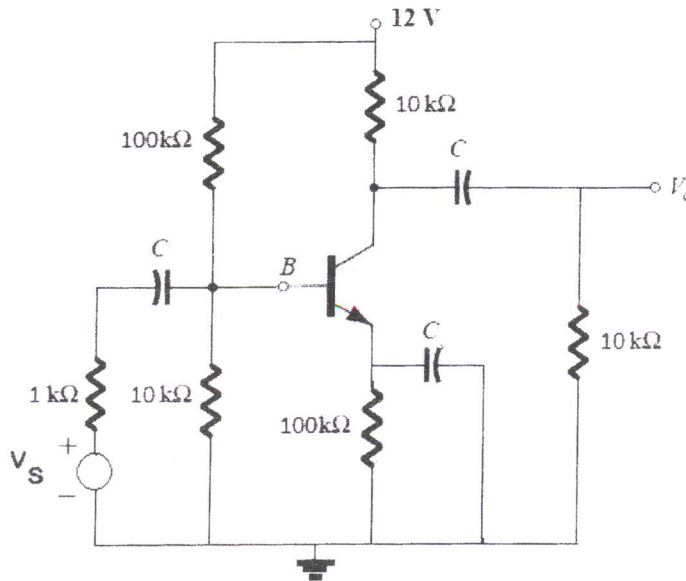


Figure 3

c] What are different coupling methods for multistage BJT amplifier? Explain them with their advantages and disadvantages. [6]

Q.4 a] A class B push pull amplifier supplies power to a resistive load of 12  $\Omega$ . The output transformer has a turns ratio of 3:1 and efficiency of 78.5%. Calculate [5]

- i) Maximum power output
- ii) Maximum power dissipation in each transistor
- iii) Maximum base and collector current for each transistor.

Assume  $h_{fe} = 25$  and  $V_{CC} = 20$  V.

b] With the help of neat diagram explain the working of class AB push pull amplifier. [3]

how negative feedback improves bandwidth of an amplifier.

- d] A negative feedback is used to reduce the noise from an amplifier by 80% [2]
- i) What must be the percentage of negative feedback to accomplish this, if the input voltage gain is 100?
  - ii) What will be the voltage gain with feedback?