

# COLLEGE OF ENGINEERING, PUNE

(An Autonomous Institute of Government of Maharashtra.)  
SHIVAJI NAGAR, PUNE - 411 005

## END Semester Examination

### (ET-207) Network Synthesis and Analog Filters

Course: B.Tech

Branch: Electronics and TeleCommunication Engineering

Semester: Sem III

Year: 2014-2015

Max.Marks:60

Duration: 3 Hours

Time:-

10 to 1.00 p.m

Date: 12/2014 DEC 2014


#### Instructions:

MIS No.

--	--	--	--	--	--	--	--	--	--


1. Figures to the right indicate the full marks.
2. Mobile phones and programmable calculators are strictly prohibited.
3. Writing anything on question paper is not allowed.
4. Exchange/Sharing of anything like stationery, calculator is not allowed.
5. Assume suitable data if necessary.
6. Write your MIS Number on Question Paper

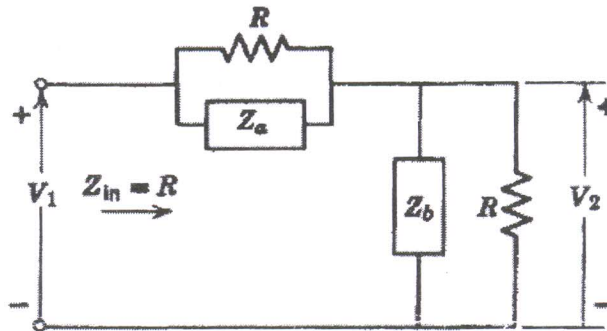Q 1 (a) For the network in the figure, show that the driving point impedance  $Z_{in}$  is equal to  $4R$  when  $Z_a \cdot Z_b = R^2$



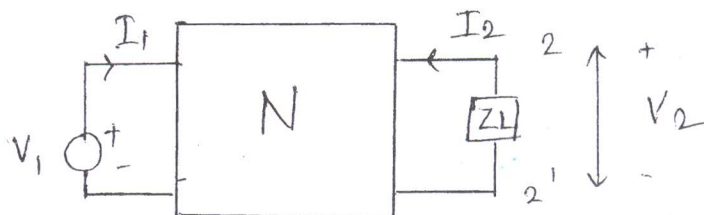(b) (i) The network N is terminated at port 2-2' with an impedance  $Z_L = \frac{1}{Y_L}$ . Show <sup>4</sup>

$$\text{that } \frac{V_2}{V_1} = \frac{-y_{21}}{y_{22} + Y_L}$$



(ii) What do you mean by reciprocal and symmetrical networks. Explain by appropriate examples.

OR

Show the response of Chebyshev Low pass Filter for N=1, N=2, N=3. Which filter approximation according to you should be preferred and why?

- (c) Explain with the help of a diagram. ANY FOUR of the following parameters of a practical Low pass Filter. 4
- (i) Cut off Frequency
  - (ii) Stop Band Frequency
  - (iii) Pass band Ripple( $\delta_p$ )
  - (iv) Stop Band Ripple( $\delta_s$ )
  - (v) Gain roll-off

**OR**

Justify the necessity of using a higher order filter (with appropriate diagrams of N=2,3... for Butterworth LPF). Obtain the transfer function of a 3<sup>rd</sup> order normalized Butterworth filter and plot the poles on the S-plane.

- Q 2 (a) (i) Let a Network Function 3

$$Z(s) = \frac{a_n s^n + a_{n-1} s^{n-1} + a_{n-2} s^{n-2} + \dots + a_1 s + a_0}{b_m s^m + b_{m-1} s^{m-1} + b_{m-2} s^{m-2} + \dots + b_1 s + b_0} = \frac{P(s)}{Q(s)}$$

Explain the basic operation of Removal of a pole at  $s = \infty$  from the function.


- (ii) What do you mean by critical frequencies? State their significance.

**OR**


- (ii) Find whether the following is RC impedance function. If yes, synthesize it in Foster 1 form.

$$Z(s) = \frac{3(s+1)(s+4)}{(s+3)}$$

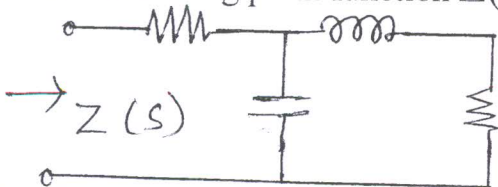- (b) Realize the driving point function  $Z(s) = \frac{s^2 + 2s + 2}{s^2 + s + 1}$  into the form shown below: 3



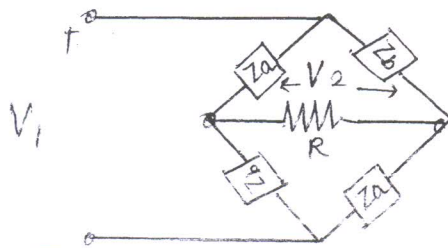- (c) What do you mean by a Constant resistance Network. Give a condition for a bridge network to be a Constant Resistance Network. 4  
Derive the Open Circuit (z) parameters for the Bridge / Lattice network shown below.




(d) Find the Transfer Function and Order N of an Equi-ripple filter having following specifications: 5

- (i) Maximum Passband Ripple ( $\delta_p$ ) = 1 dB
- (ii)  $\Omega_p = 1.2$  rad/s
- (iii) Stop band Attenuation ( $\delta_s$ ) is 40dB for  $\Omega_s = 4$  rad/s.

Q 3 (a) Synthesize the following into L-C ladder network with  $1\Omega$  termination 4

$$Z_{21} = \frac{2}{s^3 + s^2 + 4s + 2}$$

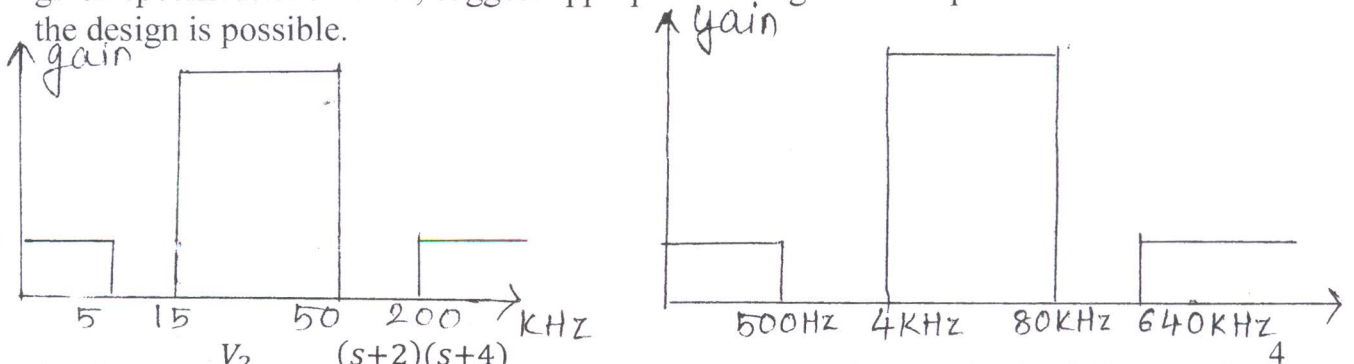
(b) State the advantages of Active Filters over Passive Filters. The Frequency Response of two Bandpass Filters is shown below. Is it possible to design the filters with the given specifications? If not, suggest appropriate changes in the specification/s so that the design is possible. 5



(c) Synthesize  $\frac{V_2}{V_1} = \frac{(s+2)(s+4)}{(s+3)(3s+4)}$  as a constant resistance bridged T-network connected in Cascade. 4


(d) (i) Illustrate with appropriate frequency response diagrams, the transformation of a passive low pass filter into band-pass filter. Derive the expressions for the cut off frequencies  $\Omega_1$  and  $\Omega_2$  of the transformed band-pass filter. 6

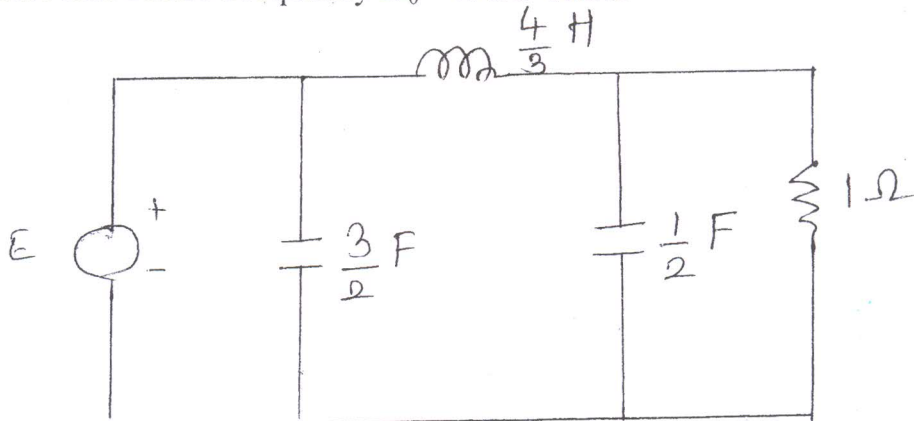(ii) Convert the LPF below into Band Stop Filter with Bandwidth  $B = 6 \times 10^4$  rad/s and centre Frequency  $\Omega_0 = 4 \times 10^4$  rad/s.



Q 4 (a) A certain low pass filter has already been designed with its magnitude characteristic  $|H_{LP}(j\Omega)|$  as shown below. 5

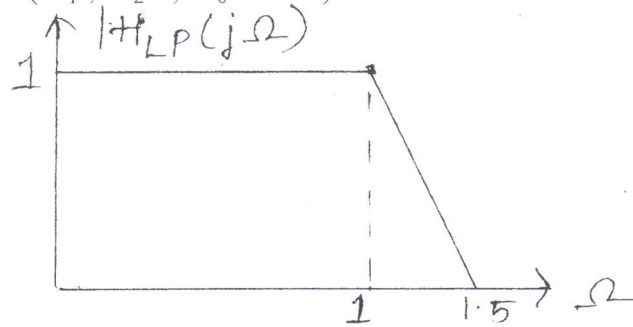The transform  $S = \frac{6s}{s^2+269}$  is applied to this function to obtain a band-reject characteristic. Give a sketch of the band-reject magnitude characteristic. Give all crucial specifications ( $\Omega_1$ ,  $\Omega_2$ ,  $\Omega_0$  and B) on this characteristic.



- (b) (i) Design a 3<sup>rd</sup> order Active Low Pass Filter with cut off frequency of 1kHz. 5  
(ii) State the significance of Quality Factor Q and Damping Factor in Filter design.
- (c) Convert a 2<sup>nd</sup> order active LPF into a HPF to get a cut off frequency of 330 Hz. 4