

College of Engineering Pune
 Electronics and Telecommunication Department
 F.Y.B.Tech.
(ET 101) Basic Electronics
 ESE (2008-2009)

Time: 3 Hour]

Instructions to candidates:


[Max. Marks: 50

- 1) **All questions in question No. 1 are compulsory.**
- 2) Attempt **any three sub-questions** from question number 2 to question number 5.
- 3) Neat Diagrams must be drawn wherever necessary.
- 4) Assume suitable data, if necessary.
- 5) Figures to the right indicate full marks.
- 6) Use of logarithmic tables and non-programmable electronic calculator is allowed.

- Q 1
- a) State fixed and adjustable voltage regulator ICs. Draw the block diagram of fixed regulator IC. (2)
 - b) Draw a diagram of half wave rectifier circuit and derive the expressions for dc voltage and r.m.s. voltage of half wave rectifier circuit. (2)
 - c) Prove the following using Boolean algebra theorems. (2)

$$\overline{A}BC + A\overline{B}C + ABC + \overline{A}B\overline{C} = AB + BC + CA$$
 - d) Draw circuit diagram of the Wien bridge oscillator. Write the expression for frequency of oscillation. (2)
 - e) Draw the block diagram of CRO. (2)
 - f) Write any four differences between frequency and amplitude modulation. (2)
 - g) Draw the circuit diagram of inverting comparator and explain the waveform. (2)
- Q 2
- a) Explain with the help of block diagram: The Public Address System (3)
 - b) What is the difference between positive logic and negative logic systems used in digital systems? (3)
 - c) With reference to the amplitude modulation scheme, draw the following waveforms: (3)
 - i. Modulation voltage,
 - ii. Carrier voltage,
 - iii. Modulated carrier wave.
 - d) Write a short note on GSM architecture. (3)

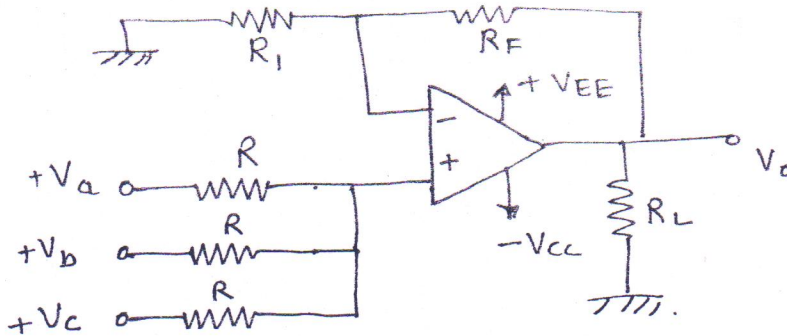- Q 3
- a) What do you mean by MOD - COUNTER? Explain the construction and working of MOD-8 asynchronous counter using suitable waveforms. (3)
- b) In the given circuit, supply voltages = ± 15 V. $V_a = +2$ V, $V_b = -3$ V, $V_c = +4$ V. $R = R_1 = 1$ K Ω and $R_F = 2$ K Ω . Determine the voltage V_1 at non inverting terminal and the output voltage V_o . Assume the OP-AMP is initially nulled. (3)



- c) Minimize the four variable logic function using K - map and realize it using NAND gates. (3)
- $$f(A, B, C, D) = ABC\bar{D} + \bar{A}BCD + \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}\bar{D} + A\bar{C} + A\bar{B}\bar{C} + \bar{B}$$
- d) Define the following terms associated with logic gates: (3)
- De-morgan Theorem
 - Race around condition
 - Undefined states of RS flip flop

- Q 4
- a) How does monostable multivibrator work? Explain with the help of detailed block diagram of 555 timer and waveforms. (3)
- b) In an astable multivibrator $R_A = 3.9$ K Ω , $R_B = 2.2$ K Ω and $C = 0.1$ μ F. Determine positive pulse width T_{ON} , negative pulse width T_{OFF} and free running frequency f_0 . (3)
- c) Define transducer. Classify transducer based on (i) Application and (ii) Electrical Principle. Give principle of working of LVDT. Specify application of it. (3)
- d) A strain gauge with a gauge factor $K = 2$ is bound to a steel member which is subjected to a strain of 10^{-6} . If the original 'no - strain' resistance of the gauge is 120 Ω , calculate the change in gauge resistance. (3)

- Q 5
- a) Why modulation is needed? Give brief classification of analog and digital modulation. (3)

- b) Derive expression for Amplitude modulated voltage. A 400 watt carrier is modulated to a depth of 75 percent. Calculate the total power in the modulated wave. (3)
- c) Derive mathematical representation of FM. Find the carrier and modulating frequencies. The modulating index and the maximum deviation of the FM wave represented by the voltage equation $v = 12 \sin(6 \times 10^8 t + 5 \sin 1250 t)$. What power will this FM wave will dissipate in 10Ω resistor? (3)
- d) Write a short note on "Wired and wireless communication". (3)
