

College of Engineering, Pune-05
F.Y.B.Tech.

Re-End Semester Examination-2008-2009
(EE101) Basic Electrical Circuits

Re-exam



Day-Thursday
Date-14/05/2008

Maximum Marks-50
Time-12.00 noon to 3.00 pm.

Instructions

- 1) All questions are compulsory.
- 2) Make necessary assumptions and assume suitable data whenever required
- 3) Only non-programmable calculators are allowed
- 4) Explain with diagram wherever necessary.
- 5) Figure to right indicate full marks.

Q.1		<p>Solve the circuit shown below in figure for all node voltages and element currents. Use nodal analysis. Verify the results obtained for element currents by mesh analysis.</p>	10														
Q.2	A	<p>A magnetic circuit comprises three parts, <i>a</i>, <i>b</i>, and <i>c</i> in series, each of which has uniform cross-sectional area. Part <i>a</i> has a length of 80mm and cross-sectional area 50 mm². Part <i>b</i> has a length of 70mm and cross-sectional area 80 mm². Part <i>c</i> is an air gap of 0.5mm in length and of cross-sectional area 60 mm². Neglecting magnetic leakage and fringing, determine the current necessary in a coil of 4000 turns wound on part <i>b</i> to produce in the air-gap a flux density of 0.7T. The magnetic characteristic for part <i>a</i> and <i>b</i> is given by:</p> <table border="1" style="margin-left: auto; margin-right: auto;"> <tbody> <tr> <td>H(A/m)</td> <td>100</td> <td>210</td> <td>340</td> <td>500</td> <td>800</td> <td>1500</td> </tr> <tr> <td>B(T)</td> <td>0.2</td> <td>0.4</td> <td>0.6</td> <td>0.8</td> <td>1.0</td> <td>1.2</td> </tr> </tbody> </table>	H(A/m)	100	210	340	500	800	1500	B(T)	0.2	0.4	0.6	0.8	1.0	1.2	05
H(A/m)	100	210	340	500	800	1500											
B(T)	0.2	0.4	0.6	0.8	1.0	1.2											
	B	<p>State the superposition theorem and use it to determine current in branch AB for the network in figure below.</p>	05														

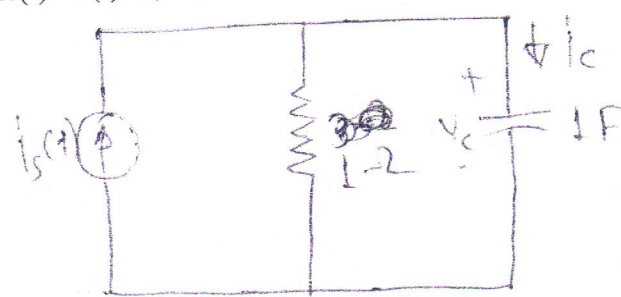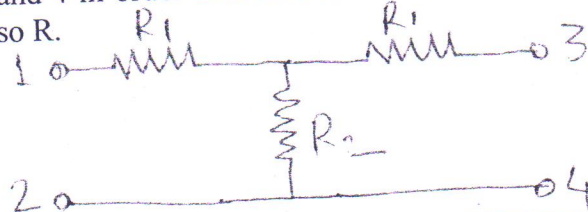C	<p>Find the voltage $V_c(t)$ and current $i_c(t)$ for the parallel RC circuit shown below in figure for the case $R=1 \text{ OHM}$, $C=1 \text{ F}$, and the applied current is the pulse $i_s(t) = u(t) - u(t-1) \text{ A}$.</p> 	05
Q.3 A	<p>Show that power consumed by three identical phase loads connected in delta is equal to three times the power consumed when the phase loads are connected in star.</p>	04
B	<p>In following figure determine the resistance R to be connected across the terminals 3 and 4 in order that the resistance measured between terminals 1 and 2 is also R.</p> 	04
C	<p>Two resistances A of 100 OHM and B of 150 OHM are connected in series. A has a resistance temperature co-efficient of $0.004 \text{ per } ^\circ\text{C}$, while the resistance temperature co-efficient of B is $0.001 \text{ per } ^\circ\text{C}$, both at 0°C. Find the resistance temperature co-efficient of combination at 0°C. Assume the values of the resistance given as at 0°C.</p>	04
D	<p>Explain the construction of DC machine with aid of neat diagram showing main parts.</p>	04
Q.4 A	<p>Calculate the line current of a three phase (star connected) alternator delivering 5 MW at 33 kV and working at 0.8 power factor.</p>	03
B	<p>Three identical resistors of 20 OHM are connected in star to a 415 V, three-phase, 50 Hz supply. (a) Calculate the power taken by the load. (b) If one of the resistor is open-circuited, calculate the power consumed.</p>	03
C	<p>A 50 kVA single-phase transformer has a turns ratio of $300/20$. The primary winding is connected to a 2200 V, 50 Hz supply. Calculate: (a) the secondary voltage on no load, (b) the approximate values of the primary and secondary currents on full load.</p>	03