

College of Engineering Pune  
 Electronics and Telecommunication Department  
 F.Y.B.Tech.  
 ( ET 101) Basic Electronics  
 ESE (2008-2009)

Time: 3 Hour]

[Max. Marks: 50

Instructions to candidates:


- 1) All questions in question No. 1 are compulsory.
- 2) Attempt any three sub-questions from question number 2 to question number 5.
- 3) Neat Diagrams must be drawn wherever necessary.
- 4) Assume suitable data, if necessary.
- 5) Figures to the right indicate full marks.
- 6) Use of logarithmic tables and non-programmable electronic calculator is allowed.

- Q 1
- a) State fixed and adjustable voltage regulator ICs. Draw the block diagram of fixed regulator IC. (2)
  - b) Draw a diagram of half wave rectifier circuit and derive the expressions for dc voltage and r.m.s. voltage of half wave rectifier circuit. (2)
  - c) Prove the following using Boolean algebra theorems. (2)  

$$\overline{A}BC + A\overline{B}C + AB\overline{C} + ABC = AB + BC + CA$$
  - d) Draw circuit diagram of the Wien bridge oscillator. Write the expression for frequency of oscillation. (2)
  - e) Draw the block diagram of CRO. (2)
  - f) Write any four differences between frequency and amplitude modulation. (2)
  - g) Draw the circuit diagram of inverting comparator and explain the waveform. (2)
- Q 2
- a) Explain with the help of block diagram: The Public Address System (3)
  - b) What is the difference between positive logic and negative logic systems used in digital systems? (3)
  - c) With reference to the amplitude modulation scheme, draw the following waveforms: (3)
    - i. Modulation voltage,
    - ii. Carrier voltage,
    - iii. Modulated carrier wave.
  - d) Write a short note on GSM architecture. (3)

Q 3 a) What do you mean by MOD-8 COUNTER? Explain the construction and working of MOD-8 asynchronous counter using suitable waveforms. (3)

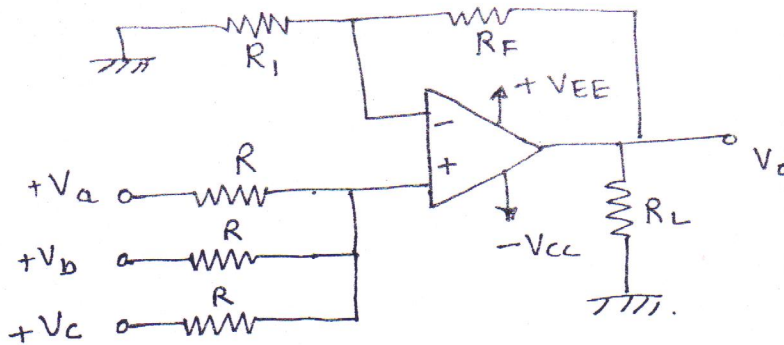b) In the given circuit, supply voltages =  $\pm 15$  V,  $V_a = +2$  V,  $V_b = -3$  V,  $V_c = +4$  V,  $R = R_1 = 1$  K $\Omega$  and  $R_F = 2$  K $\Omega$ . Determine the voltage  $V_I$  at non inverting terminal and the output voltage  $V_o$ . Assume the OP-AMP is initially nulled. (3)



c) Minimize the four variable logic function using K-map and realize it using NAND gates. (3)

$$f(A, B, C, D) = ABC\bar{D} + \bar{A}BCD + \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}\bar{D} + A\bar{C} + A\bar{B}\bar{C} + \bar{B}$$

d) Define the following terms associated with logic gates: (3)

- De-morgan Theorem
- Race around condition
- Undefined states of RS flip flop

Q 4 a) How does monostable multivibrator work? Explain with the help of detailed block diagram of 555 timer and waveforms. (3)

b) In an astable multivibrator  $R_A = 3.9$  K $\Omega$ ,  $R_B = 2.2$  K $\Omega$  and  $C = 0.1$   $\mu$ F. Determine positive pulse width  $T_{ON}$ , negative pulse width  $T_{OFF}$  and free running frequency  $f_0$ . (3)

c) Define transducer. Classify transducer based on (i) Application and (ii) Electrical Principle. Give principle of working of LVDT. Specify application of it. (3)

d) A strain gauge with a gauge factor  $K = 2$  is bound to a steel member which is subjected to a strain of  $10^{-6}$ . If the original 'no-strain' resistance of the gauge is 120 $\Omega$ , calculate the change in gauge resistance. (3)

Q 5 a) Why modulation is needed? Give brief classification of analog and digital modulation. (3)

- b) Derive expression for Amplitude modulated voltage. A 400 watt carrier is modulated to a depth of 75 percent. Calculate the total power in the modulated wave. (3)
- c) Derive mathematical representation of FM. Find the carrier and modulating frequencies. The modulating index and the maximum deviation of the FM wave represented by the voltage equation  $v = 12 \sin(6 \times 10^8 t + 5 \sin 1250 t)$ . What power will this FM wave will dissipate in  $10\Omega$  resistor? (3)
- d) Write a short note on "Wired and wireless communication". (3)

\*\*\*\*\*