



College of Engineering, Pune
End Semester Exam – May 2012
F. Y. B. Tech. (Electrical Group)
Basic Electrical Engineering EE-102





Day & Date: Sunday, 13th May 2012
 Maximum Marks: 50

Time: 9.00 am to 12.00
 Duration : 3 hrs.

Instructions:

1. All questions are compulsory and carry equal marks.
2. All questions must be attempted sequentially 1 to 5.
3. Sub-questions of each question must be attempted at one place.
4. All the symbols and notations carry their usual meaning unless otherwise stated.
5. Assume suitable data wherever necessary.

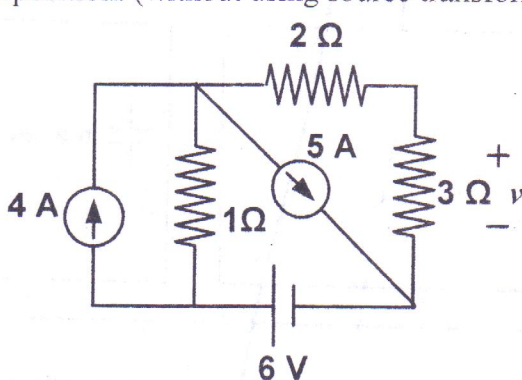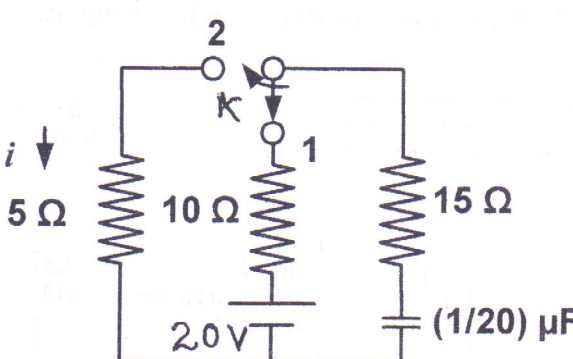Q. 1	A	<p>Find voltage v across $3\ \Omega$ resistor in the circuit shown in Figure-1A, by applying the principle of superposition. (without using source transformation).</p> <div style="text-align: center;">  <p>Figure-1A</p> </div>	5
	B	<p>In the circuit shown in Figure-1B, switch 'K' is at position 1 from long time. At $t=0$ sec, switch position is changed to 2. Find the current through $5\ \Omega$ resistor at $t=0$ sec, $t = 2\tau$ and $t = \infty$. Sketch the current waveform.</p> <div style="text-align: center;">  <p>Figure-1B</p> </div>	5

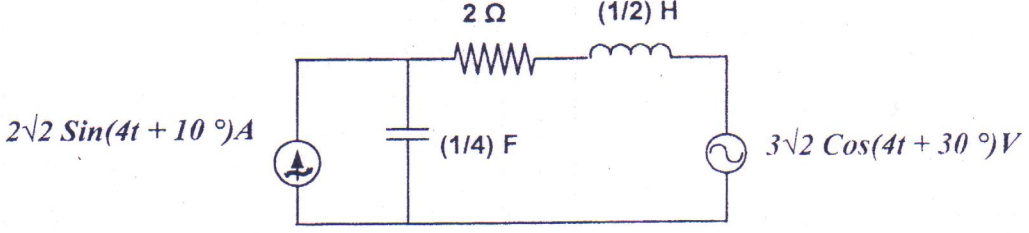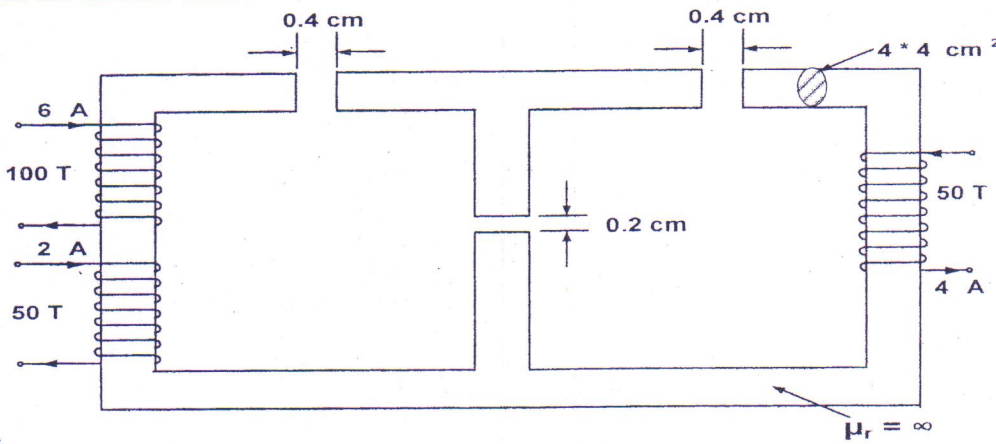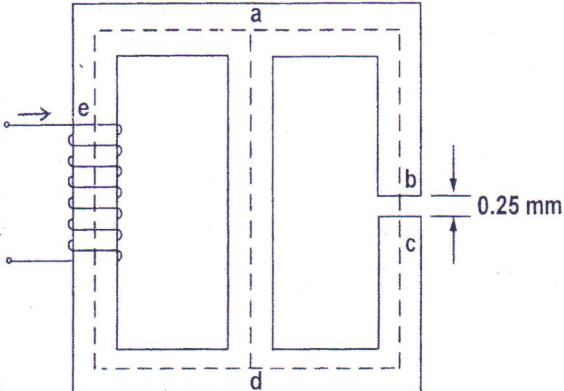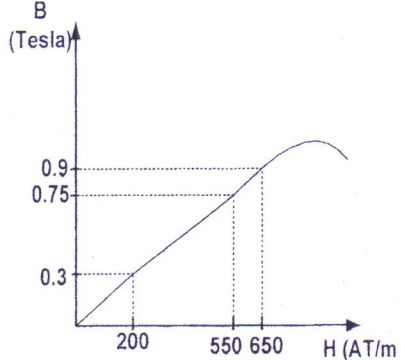Q. 2	A	<p>In the circuit shown in Figure-2A, determine the current $i(t)$ using Thevenin's theorem.</p>  <p style="text-align: center;">Figure-2A</p>	5
	B	<p>Three equivalent impedances each of $(8+j10) \Omega$ are connected in star. This is further connected to a 440 V, 50 Hz, 3-phase supply. Determine the active and reactive power and the line and phase currents.</p>	5
Q. 3	A	<p>Consider the circuit shown in the Fig. below. Find the flux density in the air-gap of the middle limb.</p> 	5
	B	<p>The magnetic circuit shown in the Fig. 3B has a cast steel core whose dimensions are given below.</p> <p>Length (ab+cd) = 100 cm, cross-sectional area = 25 cm²</p> <p>Length (ad) = 40 cm, cross-sectional area = 12.5 cm²</p> <p>Length (dea) = 100 cm, cross-sectional area = 25 cm²</p> <p>Determine the exciting coil mmf required to establish an air-gap flux of 0.75 mwb. Use B-H curve of cast steel. Neglect fringing.</p>  	5

Q. 4	A	A 40 kVA transformer with a ratio of 2000/250 V has a primary resistance of 1.15Ω and a secondary resistance of 0.01555Ω . Calculate (i) The total resistance in terms of the secondary winding (ii) Total resistance drop on full-load and (iii) Total copper loss on full-load	5
	B	The efficiency at unity power factor of a 200 kVA, 6600/600 V, single-phase transformer is 98 % both at full-load and half-load. Find the load for maximum efficiency with unity power factor. Also find the approximate current in high and low voltage winding of the transformer when it delivers this load.	5
Q. 5	A	Justify the following statements: i) Transformer is a constant flux machine ii) Fuse is a current operating protective device	4
	B	Draw circuit connection of fluorescent tube light. Explain its working.	3
	C	Why the induction motor never rotates at synchronous speed?	3