

*Elect*

**College of Engineering, Pune**  
**End Semester Exam – First Sem 2012**  
**F. Y. B. Tech. (Non Electrical Branches)**  
**(EE101)- (Basic Electrical Engineering)**



Day & Date: Sunday 2<sup>nd</sup> December 2012  
 Maximum Marks: 50

Time: 10 am to 1pm  
 Duration: 3 hrs.


**Instructions:**

1. Solve any **FIVE** questions.
2. All questions must be attempted sequentially.
3. Sub-questions of each question must be attempted at one place.
4. All the symbols and notations carry their usual meaning unless otherwise stated.
5. Assume suitable data wherever necessary.

Q. 1	A	<p>Three 60 W, 120 V light bulbs are connected across a 120 V power line as shown in figure given below. Find (i) voltage across each bulb, (ii) total power dissipation in the three bulbs.</p> <div style="text-align: center; margin: 20px 0;"> </div>	4
	B	<p>In the network shown in the figure below, the total power dissipated is 488 W. Determine the current flowing in each resistance and the potential difference between A and B.</p> <div style="text-align: center; margin: 20px 0;"> </div>	3

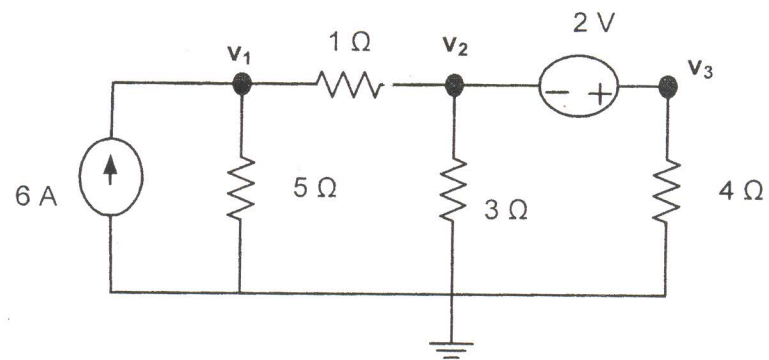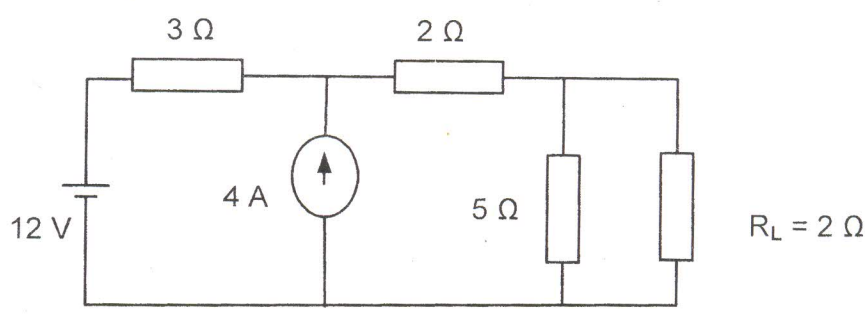	C	<p>Find the node voltages <math>v_1, v_2, v_3</math> for the circuit shown below.</p> 	3
Q. 2	A	<p>Using Norton's theorem, determine the power consumed by <math>2\ \Omega</math> resistor <math>R_L</math> in the network shown below.</p> 	5
	B	<p>A three phase delta connected load consists of three similar inductive coils, each of resistance <math>40\ \Omega</math> and inductance <math>0.35\ \text{H}</math>. The supply is <math>415\ \text{V}</math>, <math>50\ \text{Hz}</math>. Calculate (i) line current (ii) power factor (iii) total power.</p>	5
Q. 3	A	<p>Three impedances <math>Z_1 = 8 + j6\ \Omega</math>, <math>Z_2 = 4 + j3\ \Omega</math> and <math>Z_3 = 18 - j9\ \Omega</math> are connected in series across the a.c. supply. If the voltage drop across <math>Z_1</math> is <math>40 + j30</math> volts, calculate (i) current in the circuit (ii) voltage drops across <math>Z_2</math> and <math>Z_3</math> (iii) total supply voltage (iv) total power consumed by the series circuit (v) power factor of the circuit.</p>	5
	B	<p>Draw a neat diagram showing constructional details of DC machine. State function of each of the components.</p>	5
Q. 4	A	<p>A single-phase, <math>150\text{-kVA}</math>, <math>5000\text{-V}/250\text{-V}</math>, <math>50\ \text{Hz}</math> transformer has the full load copper losses of <math>1.8\ \text{kW}</math> and the core losses of <math>1.5\ \text{kW}</math>. Find (i) number of turns in each winding for a maximum core flux of <math>60\ \text{mWb}</math> (ii) efficiency at half the full load, with unity power factor.</p>	5
	B	<p>The magnetic circuit shown in figure given below has following dimensions: <math>l_1</math> (AB) = <math>10\ \text{cm}</math>, <math>l_2</math> (ACB) = <math>l_3</math> (ADB) = <math>18\ \text{cm}</math>, cross sectional area of <math>l_1</math> path = <math>6.25\ \text{cm}^2</math>, cross sectional area of <math>l_2</math> and <math>l_3</math> paths = <math>3\ \text{cm}^2</math>, length of air gap = <math>2\ \text{mm}</math>. Taking the relative permeability of the core material as <math>800</math>, find the required current in the <math>600</math> turn exciting coil so as to establish a flux of <math>100\ \mu\text{Wb}</math></p>	5

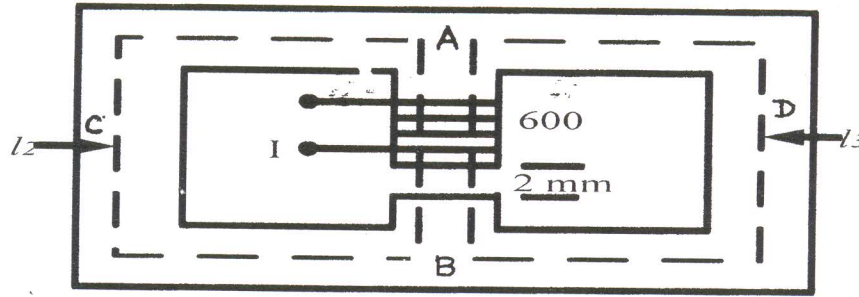in the air gap. Neglect leakage and fringing.



Q.5	A	Two coils A and B are kept, such that 70% of the flux produced by coil A links with coil B. Coil A has 11000 turns and coil B has 13000 turns. A current of 4 amp in coil A produces a flux of 0.04 mWb while a current of 4 amp in coil B produces a flux of 0.08 mWb. Calculate (i) self inductances of both the coils (ii) mutual inductance (iii) coupling coefficient.	3
	B	The resistance of copper winding of a motor at room temperature of $20^{\circ}\text{C}$ is $3.42\Omega$ . After an extended operation of the motor at full load, the winding resistance increases to $4.22\Omega$ . Find the temperature rise. Given that the temperature coefficient of copper at $0^{\circ}\text{C}$ is $0.00426/^{\circ}\text{C}$ .	4
	C	A 50 kVA, 1100/ 220 V, 50 Hz transformer has an HV winding resistance of $0.125\Omega$ and a leakage reactance of $0.625\Omega$ . The LV winding has corresponding values of $0.005\Omega$ and $0.025\Omega$ respectively. Find the equivalent impedance of the transformer referred to HV.	3
Q.6	A	With neat diagram, explain the working of fluorescent lamp.	4
	B	Answer any two of the following. (i) State laws of illumination. (ii) Compare fuse with MCB as a protective element. (iii) Explain the need of (a) grounding (b) lightning arrestor.	6

-----XXXXXX-----