



MISNO:

**COLLEGE OF ENGINEERING, PUNE**

(An Autonomous Institute of Government of Maharashtra.)

**SHIVAJI NAGAR, PUNE - 411 005**

**End Semester Examination**

**(CT-202) Digital Systems**

**Course: B.Tech  
Semester - III  
Year:2014-15  
Duration:3 hrs**

**Branch:I.T- Comp Engg.**

**Max. Marks: 60  
Date: 26/11/2014**

**Time :10:00-1:00 p.m**

**Instructions:**

1. Figures to the right indicate the full marks.
2. Mobile phones and programmable calculators are strictly prohibited.
3. Writing anything on question paper is not allowed.
4. Exchange/Sharing of anythings like stationery, calculator is not allowed.
5. Assume suitable data if necessary.
6. Write your MIS Number on Question Paper
7. Write answers for each section in separate answer sheets provided.

Q1 a Explain in details what do you understand by PLD's. Write short note on PLA 5 m

A combinational circuit is defined by the function-

$$F1(A,B,C)=\sum(3,5,6,7)$$

$$F2(A,B,C)=\sum(0,2,4,7)$$

Implement the circuit with a PLA having 3 inputs, 4 product terms, and two outputs.

Q1 b Explain with logic diagram clocked RS Flip-Flop using four NAND gates and D- flip-flop with AND and NOR gates. 5 m

OR

Explain in detail Static RAM memory cell.

5 m

Draw timing diagram for WRITE cycle for static RAM cell.

- Q2 Use the QM Method for minimization and find expression for following function  $F(A,B,C,D) = \sum M(0,1,2,3,5,7,8,9,11,14)$  10 m
- Q3 Explain the SISO Register design for input data string 1010 with the neat logic diagram. Draw corresponding waveforms for its functioning. 10 m

### Section B

- Q4 Design a synchronous counter that counts 000,010,101,110,000,010..... 10 m  
Ensure that the unused states of 001,011,100 and 111 go to 000 on next clock pulse.

Use JK-flipflops for designing the counter.

What will be the modulus of the counter?

How will the counter look like if unused states are to be considered as don't care conditions.

- Q5 What do you understand by Shift register counter. Describe 4-bit Circulating counter in detail with waveforms. Determine the number of flipflops required to construct- 10 m

a. Mod-10 Ring counter

b. Mod-10 Johnson counter

c. State the count sequence in both cases (a) and (b)

- Q6 Draw ASM chart, state table and state diagram for synchronous circuit. The circuit has control input 'C' clock and outputs as x,y,z. 10 m

If C=1, on every clock rising edge the code on output x,y & z changes from 000--->010--->100--->110--->000 and repeats.

If C=0 circuit holds present state.

Write short note on ASM.

OR

- Q6 What is VHDL? Write VHDL code for SR latch using NAND gates. 10 m