



COLLEGE OF ENGINEERING, PUNE

(An Autonomous Institute of Government of Maharashtra.)
SHIVAJI NAGAR, PUNE - 411 005

END Semester Examination

(IE-205) Electrical Measurement and Instrumentation

Course: B.Tech

Branch: Instrumentation and Control Engineering

Semester: Sem III

Year: 2014-2015

Max.Marks:60

Duration: 3 Hours

Time:- 10.00 to 1.00 p.m

Date:- 28 NOV 2014

Instructions:

MIS No.

--	--	--	--	--	--	--	--	--	--

1. Figures to the right indicate the full marks.
2. Mobile phones and programmable calculators are strictly prohibited.
3. Writing anything on question paper is not allowed.
4. Exchange/Sharing of anything like stationery, calculator is not allowed.
5. Assume suitable data if necessary.
6. Write your MIS Number on Question Paper

- Q. 1 A A signal is coming at the rate of 72 pulses/min. Design a digital instrument to measure and display frequency of this signal. 10
- B Temperature sensor is placed to measure temperature of rocket engine. Design a complete system to control reverse counter at the time of rocket launching with respect to engine temperature. (Sensor used is pt1000 (1000 ohms at 0 °C and 138.4 ohms at 1000 °C), temperature set point 450°C). 10
- C State the importance of Q-factor measurement. Also state the method for tuning the Q-meter. 5
- Q. 2 A Define resolution of ADC. What should be resolution of ADC for the following conditions? (Given:- V_{ref+} is 5V and V_{ref-} is 0V)
- a) Input analog voltage range is 0V to 2.25V and min change that should be detected is 4mv.
- b) Input analog voltage range is 1.5V to 2.5V and min change that should be detected is 1mv.
- B Design a signal generator for following specifications:- 5
- 1) Frequency 100KHz to 10MHz
- 2) Output waves:-sine
- Output voltage level(variable) $\pm 12V$
- C Derive balanced Kelvin's double bridge equation. 5

- A A $500\mu\text{A}$ meter movement with an internal resistance of 50Ω is to be converted into a 0-1mA and 0-2V. Calculate the value of shunt resistance and series resistance required. What is sensitivity of the meter?
- B What is total harmonic distortion? Explain fundamental suppression analyzer with the help block diagram.
- C Write a short note on Arbitrary function generator.
- D Design a shunt type ohmmeter. The movement to be used requires 0.5mA for full scale deflection and has an internal resistance of 50Ω . The internal battery has a voltage of 1.5V. The desired value of full scale resistance is $10\text{K}\Omega$. Calculate the values of shunt resistance.
- E Derive balanced equation of Maxwell bridge. List any four applications of Maxwell bridge.
- F Explain working of electrodynamicometer as wattmeter.