



COLLEGE OF ENGINEERING, PUNE

(An Autonomous Institute of Government of Maharashtra.)
SHIVAJI NAGAR, PUNE - 411 005

END Semester Examination

(ET-501) Power Electronics and Drives

Course: M.Tech

Branch: Mechatronics

Semester: Sem I

Year: 2014-2015

Max.Marks:60

Duration: 3 Hours Time:- ---2.00pm To 5.00 pm

Date:--24/11/14

Instructions:

MIS No.

--	--	--	--	--	--	--	--	--	--

1. Solve any 6 questions
2. Figures to the right indicate the full marks.
3. Mobile phones and programmable calculators are strictly prohibited.
4. Writing anything on question paper is not allowed.
5. Exchange/Sharing of anything like stationery, calculator is not allowed.
6. Assume suitable data if necessary.
7. Write your MIS Number on Question Paper

- Q.1 a) Describe different modes of operation of thyristor with help of V-I characteristics Explain turn on and turn off characteristics of SCR in detail with relevant waveforms of anode voltage, anode current, power loss 6
- b) Differentiate BJT and IGBT 4
- Q.2 a) Draw schematic of 1 phase full converter bridge with RLE load. Explain its working with relevant waveforms of input voltage output voltage and output current 5
- b) Compare circulating and non circulating mode dual converter 5
- Q.3 a) Draw circuit schematic of a bridge type cyclo converter and explain how one circuit can be used as step up and step down frequency converter along with wave forms 8
- b) Enlist the types of DC drives 2
- Q.4 a) Explain working of AC voltage controller with RL load 5
- b) Explain construction of Power Mosfet and the switching performance with relevant waveforms. Indicate clearly turn on and turn of components 5

- Q.5) Discuss the principle of working of three phase bridge inverter with an appropriate circuit diagram. Draw phase and line voltage waveforms on assumption that each thyristor conducts for 180° and resistive load star connected . The sequence of firing of various SCRs should also indicated in the diagram 10
- Q.6) a) Explain working of 1phase full converter DC drive with circuit schematic and waveforms of input output voltages and output current and source current 5
- b) Explain any one method of chopper control Dc drive. Derive the necessary equations What is the condition to use copper control for regenerative control 5
- Q.7 a) A 220 V,1500 rpm 10A separately excited dc motor has an armature resistance of 1 ohm. It is fed from a single phase fully controlled bridge rectifier with an ac source voltage of 230V,50 Hz. Assuming continuous load current , compute 6
- 1) Motor speed at the firing angle of 40° and torque of 7 Nm
 - 2) Developed torque at the firing angle of 45° and speed 1000 rpm
- b) A DC chopper is used for used for regenerative braking of separately excited dc motor. The dc supply voltage is 380 V. The motor has $R_a= 0.2\Omega$, $K_m=1.2V\text{-s/rad}$. The average armature current during regenerative braking is kept constant at 300A with negligible ripple 4
- For duty cycle of 60% for a chopper, Determine
- 1) minimum and maximum permissible braking speed
 - 2) speed during regenerative braking